

# CSCE 22104

## Lab Report

---

Brent Marcus Orlina

ID: 011019116

Lab Section 001

Lab 6

## Introduction

This lab's goal was to create a 1-bit ALU component and create a 16-bit ALU component, using 1-bit components. The ALU components should support four operations: addition, subtraction, logical-and, and logical-or, using the opcodes 00, 01, 10, and 11, respectively. The components should also be asynchronous, i.e. the component does not depend on a clock.

## Approach

```
1  entity ALU1Bit is
2      port(
3          s : in std_logic_vector(1 downto 0);
4          a : in std_logic;
5          b : in std_logic;
6          cin : in std_logic;
7          sout : out std_logic;
8          cout : out std_logic
9      );
10 end ALU1Bit;
```

Listing 1: The 1-bit ALU component's ports.

The 1-bit ALU component was first implemented. Listing 1 shows the ports that the ALU takes in. The input port **s** represents the opcode, determining whether the ALU should execute an addition, subtraction, logical-and, or logical-or operation. The input ports **a** and **b** are the operands. The input port **cin** is the carry-in from a previous ALU component, used for the addition and subtraction operations. It is unused when performing a logical-and or a logical-or operation.

The output port **sout** is the result of the operation that was executed. Output port **cout** is used for addition and subtraction operations, connected to the next ALU component so that it can correctly calculate the result. Although **cins** and **couts** are not used for the logical-and and logical-or operations, it will still be calculated regardless. It will not affect the result since the two logical operations do not use the **cin** input port.

```

1 architecture Datapath of ALU1Bit is
2     signal inverse_b : std_logic;
3     signal sout_adder : std_logic;
4     signal sout_and : std_logic;
5     signal sout_or : std_logic;
6 begin
7     inverse_b <= b xor s(0);
8
9     sout_adder <= a xor inverse_b xor cin;
10    sout_and <= a and b;
11    sout_or <= a or b;
12
13    sout <= sout_adder when s(1) = '0' else
14           sout_and when s = "10" else
15           sout_or when s = "11";
16    cout <= (a and inverse_b) or (cin and a) or (cin and inverse_b);
17 end Datapath;

```

Listing 2: The 1-bit ALU component's datapath implementation.

Listing 2 shows the implementation for each of the operations that the ALU supports. Firstly, the signals `sout_adder`, `sout_and`, and `sout_or`, correspond to the results of each operations that the ALU supports, with `sout_adder` corresponding to both the addition and subtraction operations. The signal `inverse_b` is used to support subtraction. The results of all of the operations are calculated with the input port `s` deciding which result to connect to the output port `sout` by using the operations' respective opcodes.

Notice that since the result of addition and subtraction operations both correspond to only one signal. This allows it so that only the 1<sup>st</sup> bit is checked to be a 0 since both operations' opcodes have their 1<sup>st</sup> as a 0. The motivation behind merging both operations into one signal is that binary subtraction in twos complement is equivalent to

$$A - B = A + (\tilde{B} + 1) \quad (1)$$

therefore, the input port `b` must simply be inverted to support the subtraction operation. Since the addition and subtraction's opcodes are different in the 0<sup>th</sup> bit where subtraction has a 1, `b` can simply be XORed by the 0<sup>th</sup> bit of the opcode, which inverses `b` when the opcode signals for a subtraction operation. This potential inverse of `b` is connected to the `inverse_b` signal, used only by the addition and subtraction operations, so that it does not affect the other operations in which the 0<sup>th</sup> bit of the opcode is a 1.

The addition of the extra 1 to  $\tilde{B}$  in 1 is not implemented in the 1-bit ALU since if the 16-bit ALU was implemented using sixteen 1-bit ALUs, it would add an extra 1 in each bit of the 16-bit ALU, producing the wrong result. The extra 1 will come from the `cin` of the first 1-bit ALU, again using the  $0^{th}$  bit of the opcode, later shown in [REF to later figure here].

The addition operation remains correct as the input port `b` won't be inverted and there won't be an extra addition of one since the  $0^{th}$  bit of the opcode will be 0. The other two operations, logical-and and logical-or, are trivial by simply performing an AND or an OR between input ports `a` and `b`. The `cout` output port is also somewhat trivial, implemented similarly to a normal Full Adder. However, it uses the signal `inverse_b` to support subtraction.

```

1  entity ALU16Bit is
2      port(
3          s : in std_logic_vector(1 downto 0);
4          a : in std_logic_vector(15 downto 0);
5          b : in std_logic_vector(15 downto 0);
6          sout : out std_logic_vector(15 downto 0);
7          cout : out std_logic
8      );
9  end ALU16Bit;
10

```

Listing 3: The 16-bit ALU component's ports.

Now that the 1-bit ALU has been implemented, the 16-bit ALU can now be constructed using sixteen 1-bit ALU components. Listing 3 shows the 16-bit ALU component's ports. Notice that the input ports `a` and `b` and the output port `sout` are now `std_logic_vectors` with 16 bits each, since the data will be 16 bits long. The input port `s` is unchanged as it still corresponds to the opcode. The output port `cout` also remains unchanged as it will be the `cout` of the last 1-bit ALU component.

```

1  architecture Datapath of ALU16Bit is
2      component ALU1Bit
3          port(
4              s : in std_logic_vector(1 downto 0);
5              a : in std_logic;
6              b : in std_logic;
7              cin : in std_logic;
8              sout : out std_logic;
9              cout : out std_logic
10         );
11     end component;
12     signal carry : std_logic_vector(14 downto 0);
13 begin
14     bit0 : ALU1Bit port map(s, a(0), b(0), s(0),      sout(0),  carry(0) );
15     bit1 : ALU1Bit port map(s, a(1), b(1), carry(0),  sout(1),  carry(1) );
16     bit2 : ALU1Bit port map(s, a(2), b(2), carry(1),  sout(2),  carry(2) );
17     bit3 : ALU1Bit port map(s, a(3), b(3), carry(2),  sout(3),  carry(3) );
18     bit4 : ALU1Bit port map(s, a(4), b(4), carry(3),  sout(4),  carry(4) );
19     bit5 : ALU1Bit port map(s, a(5), b(5), carry(4),  sout(5),  carry(5) );
20     bit6 : ALU1Bit port map(s, a(6), b(6), carry(5),  sout(6),  carry(6) );
21     bit7 : ALU1Bit port map(s, a(7), b(7), carry(6),  sout(7),  carry(7) );
22     bit8 : ALU1Bit port map(s, a(8), b(8), carry(7),  sout(8),  carry(8) );
23     bit9 : ALU1Bit port map(s, a(9), b(9), carry(8),  sout(9),  carry(9) );
24     bitA : ALU1Bit port map(s, a(10), b(10), carry(9),  sout(10), carry(10));
25     bitB : ALU1Bit port map(s, a(11), b(11), carry(10), sout(11), carry(11));
26     bitC : ALU1Bit port map(s, a(12), b(12), carry(11), sout(12), carry(12));
27     bitD : ALU1Bit port map(s, a(13), b(13), carry(12), sout(13), carry(13));
28     bitE : ALU1Bit port map(s, a(14), b(14), carry(13), sout(14), carry(14));
29     bitF : ALU1Bit port map(s, a(15), b(15), carry(14), sout(15), cout    );
30 end Datapath;
31

```

Listing 4: The 16-bit ALU component's datapath implementation.

Listing 4 shows the implementation of the 16-bit ALU component, using a sixteen 1-bit ALU components. The opcode, in the input port `s`, is connected to all of the 1-bit ALU components since each 1-bit ALU component needs to know the operation to execute. Each bit of the input ports `a` and `b` as well as the output port `sout` are connected to the corresponding 1-bit ALU component.

To make the addition and subtraction operations work correctly, a 1-bit ALU component's `cout` output port must be connected to the next 1-bit ALU component's `cin` input port, acting as the carry. The last 1-bit ALU component's `cout` output port is connected to the 16-bit ALU component's `cout`. The first 1-bit ALU component's `cin` is connected to the 0<sup>th</sup> bit of the opcode. This is because if the operation to be executed is subtraction, which has the opcode of 01, must have an extra 1 added as shown in equation 1. If the operation is addition, the opcode would be 00, thus not adding an extra 1, correctly calculating the result. The other two operations do not

use the `cin` and `cout` ports, correctly calculating the results bit by bit.

## Experimentation

Both components were individually tested using a testbench. The 1-bit ALU component was tested by going through all of the operations, each with all possible combinations of the input ports `a`, `b` and `cin`. The 16-bit ALU component was tested with a given list of inputs and manually verifying that the outputs are correct.

## Results & Discussion

 


Figure 1: The waveform for the 1-bit ALU component.

The 1-bit ALU component works as expected. Figure 1 shows the waveform of the 1-bit ALU component, correctly outputting the results of each operation. For the subtraction operation, it is noteworthy that the output is unintuitive, especially shown when the signals `A`, `B`, and `CarryIn` are all zeroes while the output shows the signal `Sum` to be active. This is because `B` is being inverted and then being "added" to zeroes, resulting in `Sum` to be active. Though the implementation results in this peculiarity, it is required for the 16-bit ALU to work.

 


Figure 2: The waveform for the 16-bit ALU component. Signals that display a blank are zeroes.

The 16-bit ALU component works as expected. Figure 2 shows the waveform of the 16-bit ALU component, correctly outputting the results of each operation. The waveform also displays the signal `OpCode` in signed decimal, with the signals `-2` and `-1` corresponding to the opcodes `10` and `11` respectively. Table 1 shows the waveform results in table form.

S1	S0	A	B	Sout	Cout
0	0	100	230	330	0
0	0	-20	60	40	1
0	0	1	1	2	0
0	1	500	340	160	1
0	1	55	70	-15	0
0	1	-1	14	-15	1
1	0	128	512	0	0
1	0	3000	2	0	0
1	0	5342	978	210	0
1	1	16	8	24	1
1	1	0	2345	2345	0
1	1	-1	5	-1	1

Table 1: Results of the 16-bit ALU component testbench in table form.

## Conclusions

Both the 1-bit ALU and 16-bit ALU components worked correctly and displayed the expected behavior during testing. The knowledge learned from this lab was learning how to construct 1-bit ALU component that handled multiple operations determined by an opcode. Learning how subtraction works in binary was also a part of the lab, as well as learning how to construct a 16-bit ALU component using out of 1-bit ALU components.